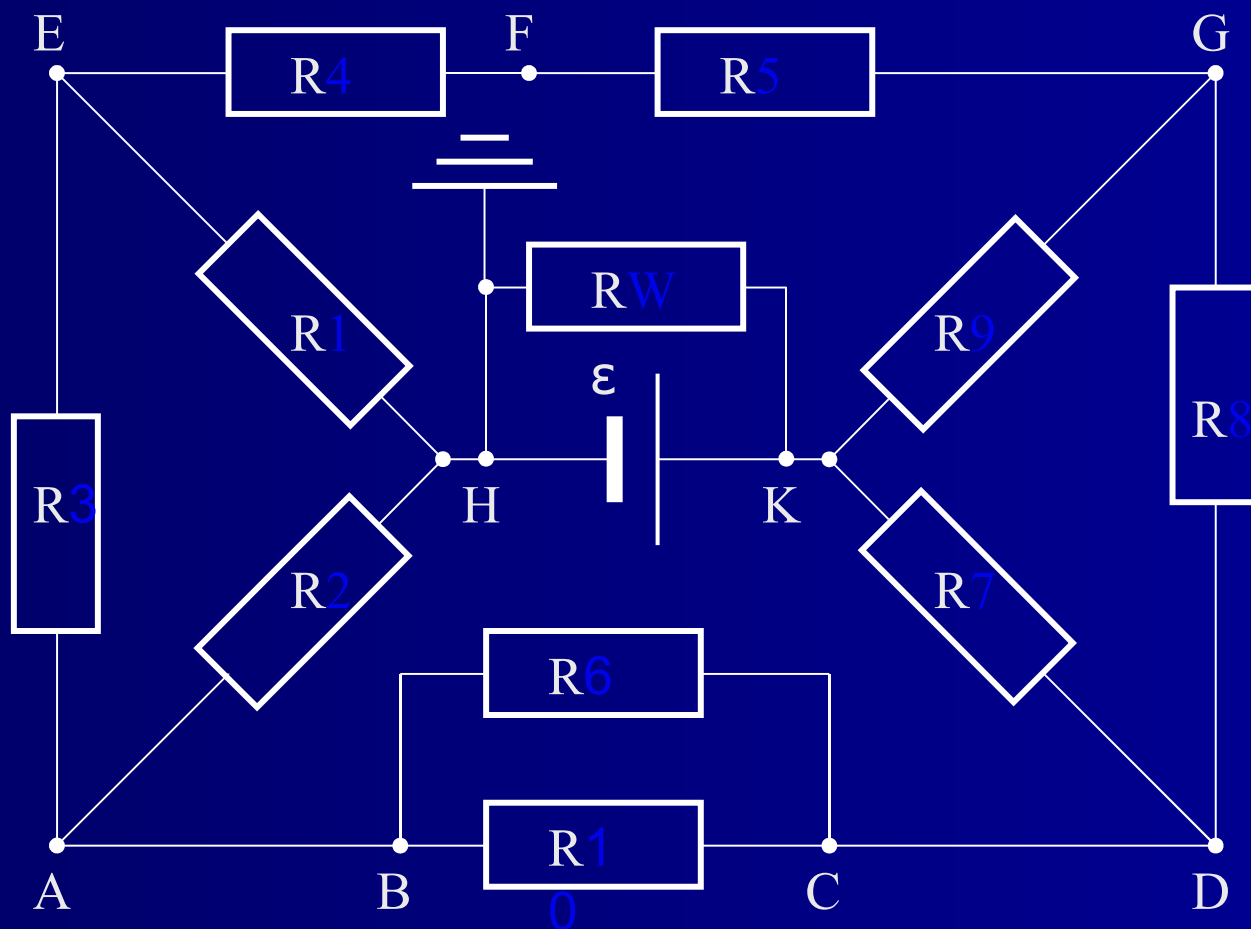


Ćwiczenie 11



Ćwiczenie 11

Dane obwodu:

$$R_1 = 6 \text{ } [\Omega]$$

$$R_2 = 3 \text{ } [\Omega]$$

$$R_3 = 4 \text{ } [\Omega]$$

$$R_4 = 8 \text{ } [\Omega]$$

$$R_5 = 12 \text{ } [\Omega]$$

$$R_6 = 9 \text{ } [\Omega]$$

$$R_7 = 15 \text{ } [\Omega]$$

$$R_8 = 10 \text{ } [\Omega]$$

$$R_9 = 5 \text{ } [\Omega]$$

$$R_{10} = 9 \text{ } [\Omega]$$

$$R_w = 2 \text{ } [\Omega]$$


$$\varepsilon = 20 \text{ } [V]$$

Ćwiczenie 11

Oblicz potencjał względem masy punktów:
A, B, C, D, E, F, G, H, K

Oblicz różnicę potencjałów między
punktami: AF, BG, DE

Ćwiczenie 11

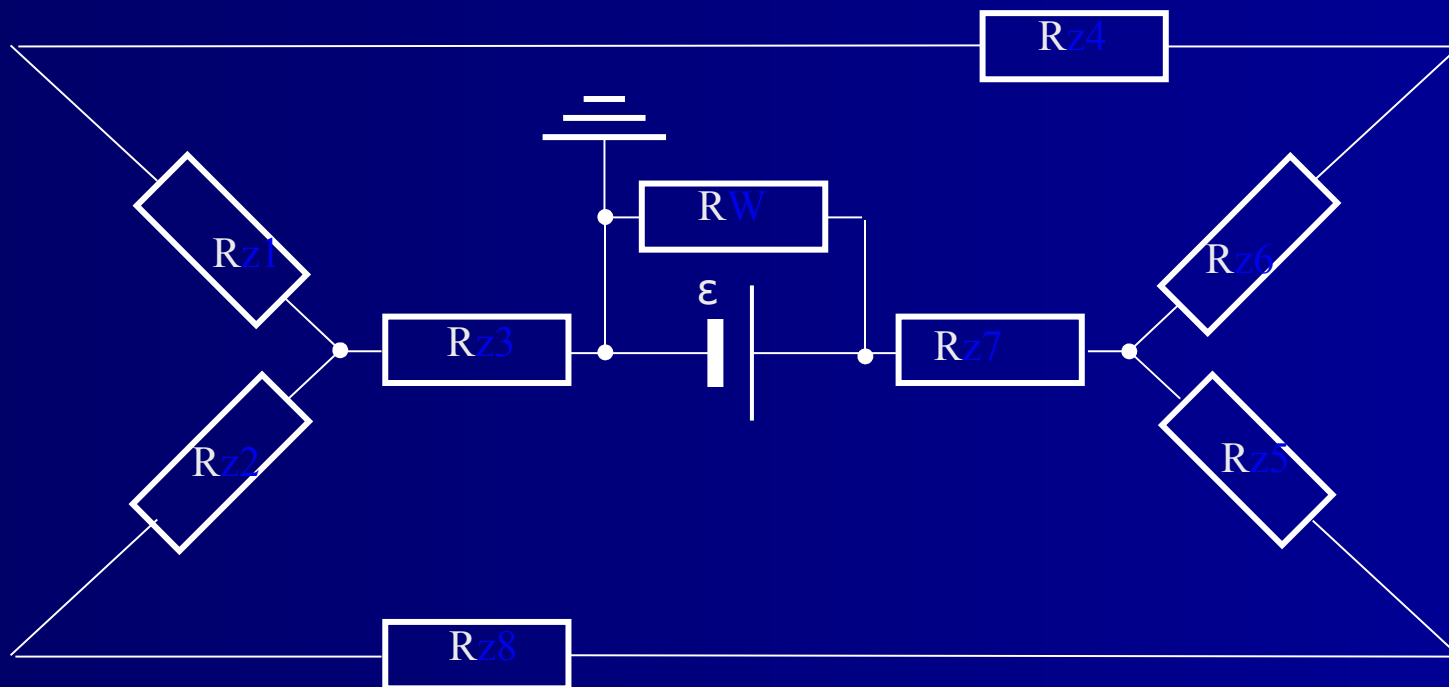

Ćwiczenie 11

$$R_{z1} = \frac{R_1 \cdot R_3}{R_1 + R_2 + R_3} = \frac{6[\Omega] \cdot 4[\Omega]}{6[\Omega] + 3[\Omega] + 4[\Omega]} = 1,85[\Omega]$$

$$R_{z2} = \frac{R_3 \cdot R_2}{R_1 + R_2 + R_3} = \frac{4[\Omega] \cdot 3[\Omega]}{6[\Omega] + 3[\Omega] + 4[\Omega]} = 0,92[\Omega]$$

$$R_{z3} = \frac{R_2 \cdot R_1}{R_1 + R_2 + R_3} = \frac{3[\Omega] \cdot 6[\Omega]}{6[\Omega] + 3[\Omega] + 4[\Omega]} = 1,38[\Omega]$$

Ćwiczenie 11

$$R_{z5} = \frac{R_7 \bullet R_8}{R_7 + R_8 + R_9} = \frac{15[\Omega] \bullet 10[\Omega]}{15[\Omega] + 10[\Omega] + 5[\Omega]} = 5,0[\Omega]$$

$$R_{z6} = \frac{R_8 \bullet R_9}{R_7 + R_8 + R_9} = \frac{10[\Omega] \bullet 5[\Omega]}{15[\Omega] + 10[\Omega] + 5[\Omega]} = 1,67[\Omega]$$

$$R_{z7} = \frac{R_9 \bullet R_7}{R_7 + R_8 + R_9} = \frac{5[\Omega] \bullet 15[\Omega]}{15[\Omega] + 10[\Omega] + 5[\Omega]} = 2,5[\Omega]$$

Ćwiczenie 11


$$R_{z4} = R_4 + R_5 = 8[\Omega] + 12[\Omega] = 20[\Omega]$$

$$\frac{1}{R_{z8}} = \frac{1}{R_6} + \frac{1}{R_{10}}$$

$$R_{z8} = \frac{R_6 \cdot R_{10}}{R_6 + R_{10}}$$

$$R_{z8} = \frac{9[\Omega] \cdot 9[\Omega]}{9[\Omega] + 9[\Omega]} = 4,5[\Omega]$$

Ćwiczenie 11

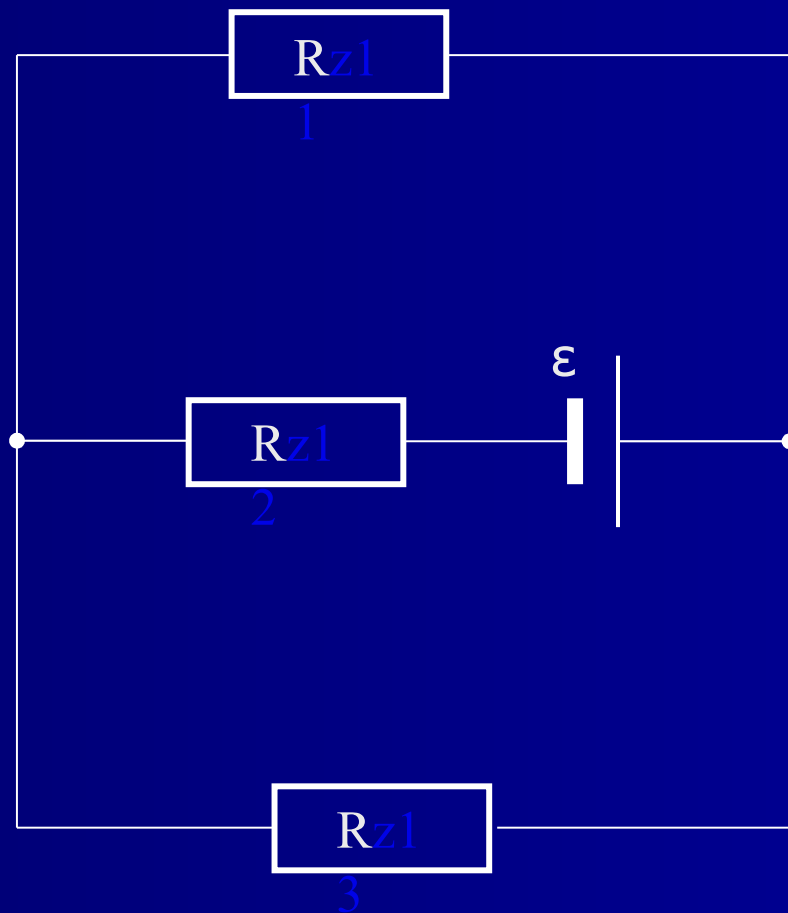

Ćwiczenie 11

$$R_{z11} = R_{z1} + R_{z4} + R_{z6} = 1,85[\Omega] + 20[\Omega] + 1,67[\Omega]$$

$$R_{z11} = 23,51[\Omega]$$

$$R_{z12} = R_{z3} + R_W + R_{z7} = 1,38[\Omega] + 2[\Omega] + 2,5[\Omega]$$

$$R_{z12} = 5,88[\Omega]$$

$$R_{z13} = R_{z2} + R_{z8} + R_{z5} = 0,92[\Omega] + 4,5[\Omega] + 5[\Omega]$$

$$R_{z13} = 10,24[\Omega]$$


Ćwiczenie 11

$$\frac{1}{R_{z10}} = \frac{1}{R_{z11}} + \frac{1}{R_{z13}}$$


$$R_{z10} = \frac{R_{z11} \cdot R_{z13}}{R_{z11} + R_{z13}}$$

$$R_{z10} = \frac{23,51[\Omega] \cdot 10,42[\Omega]}{23,51[\Omega] + 10,42[\Omega]}$$

$$R_{z10} = 7,22[\Omega]$$

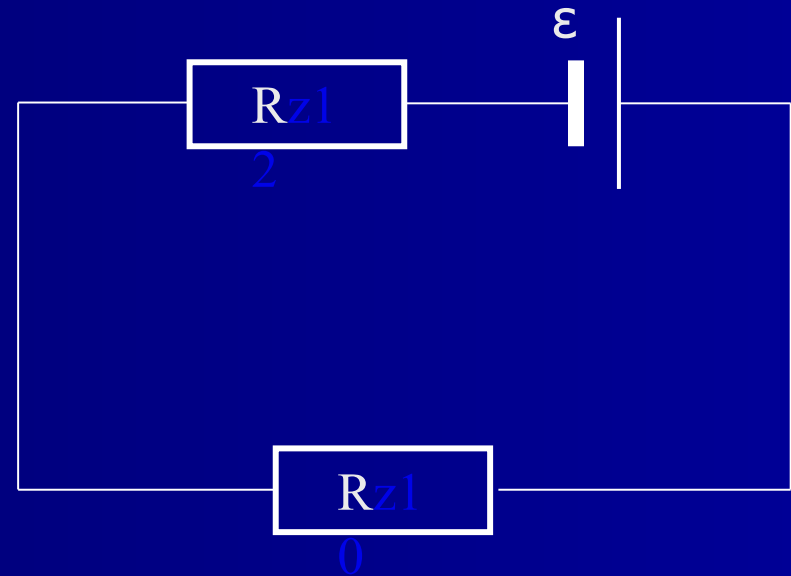

Ćwiczenie 11

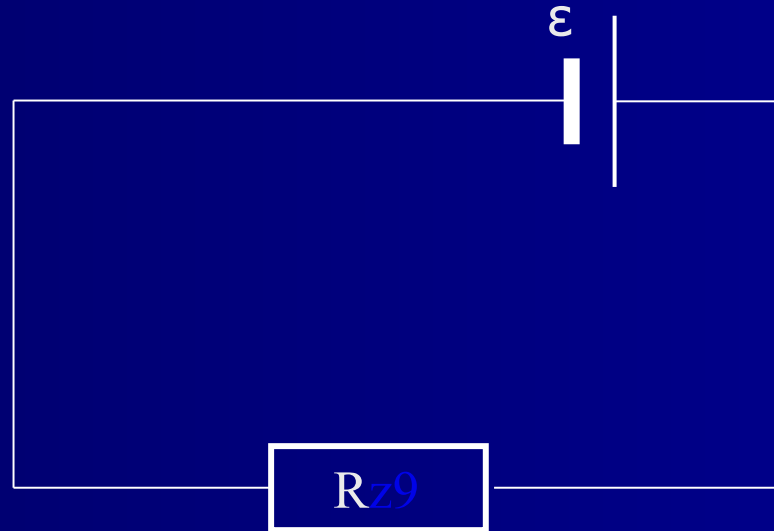

$$R_{z9} = R_{z12} + R_{z10} = 5,88[\Omega] + 7,22[\Omega] =$$

$$R_{z9} = 13,1[\Omega]$$

$$i_9 = \frac{\varepsilon}{R_{z9}} = \frac{20[V]}{13,1[\Omega]} = 1,526[A]$$

Ćwiczenie 11

